

Do-It-Yourself Crystal Diodes

Mt. Beacon Amateur Radio Club
17 June 2008

Ed Nisley - KE4ZNU
ed.nisley@ieee.org

1-33

Coming Attractions

Radio Rocks
EZ Curve Tracer
AM Radio Circuit Model
Minerals: Diodes & Thingies
Rust Never Sleeps
Why Diodes Matter

2-33

In The Beginning


- Before integrated circuits...
- Before transistors...
- Before vacuum tubes...
- Before *electronics*...
- ... there were radios!
- Modern crystal radio by VEGAB



3-33

The Simplest Possible Radio

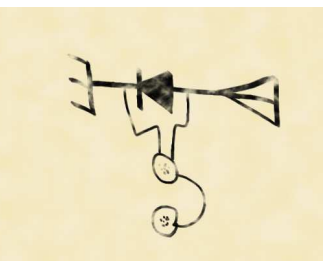- Antenna
- Ground
- Earphone
- Detector
- AM demodulator (huh?)
- A rock on a hard place
- Crystal diode!
- Tuning? *Bah!*



4-33

Mineral Samples


- Who knew?
- Nobody!
- Conflicting stories
- Try all combinations
- Most don't work
- How can you tell?
- Instrumentation
- Numbers = science!



5-33

The Big Idea

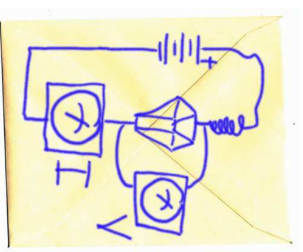
- Jam current (I) in
- How much?
- Polarity?
- Measure volts (V) across
- Range?
- Plot results: curves!
- It can be done manually
- *Much* more fun automatically
- Oscilloscope screen shots



6-33


The Little Details

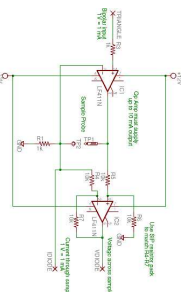- Triangle wave input
- 200 Hz, 8 V peak
- Voltage to Current
- Oscilloscope X axis
- Measure V at sample
- Differential to single
- Oscilloscope Y axis
- ± 10 mA and ± 10 V
- Makes it'sy sparks...



7-33

Enlarged to Show Texture

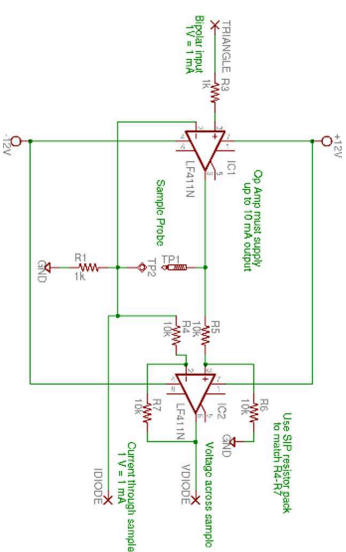

8-33

Cat's Whisker Probe


- Mineral in metal pot
- Pin-point probe
- Steel? Bronze? Carbon?
- 3-axis ball+slide mount
- Springy contact thing
- Patience?
- Patience...
- Patience!



9-33

He Who Dies With The Most Stuff...

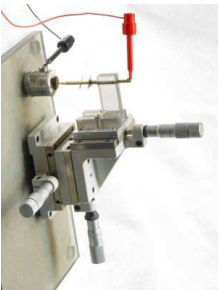- 3-axis linear positioner
- 0.001" resolution
- 0.5" accessible cube
- Zero backlash
- Black-belt dweebdom
- But if you have one...



10e33

Probe and Sample Holder

- Telescoping brass tubes
- Tapered clock pins
- Springy thing
- Friction-fit probe tips
- Steel, bronze, carbon...
- Low frequency means clip leads work fine



11e33

Sample Holder


- EMT fitting "cup"
- Al foil padding
- Wood's Metal
- Solid contact
- Melts at 160° F
- But: **Pb+Cd+Bi+Sn**
- Field's Metal = 144° F
- Cerrosafe = 165° F
- See that hole?



12e33

Calibration – 1 kΩ Resistor

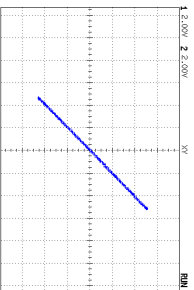
- 1 V / in = 1 mA out
- Slope = resistance
- Set Scope Axes
- X = current (2 mA/div)
- Y = voltage (2 V/div)
- Linear!
- Whew...
- Tweak DC offset = 0



13e33

Calibration – 1N914

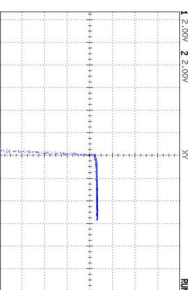
- Jellybean Si diode
- $V_{fwd} = 0.5$ V
- Pretty close
- $I_{rev} = zilch$
- Limited by diff amp's input resistance
- A *nearly* ideal diode



14e33

Iron Pyrite

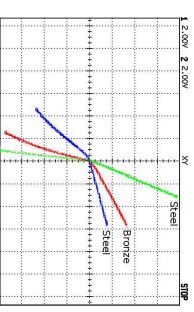
- Green trace
- Nearly a resistor
- Red trace
- Almost a diode
- Blue trace
- Better & worse
- Same lump!
- Does probe really matter?



15e33

Spice Model of AM Radio

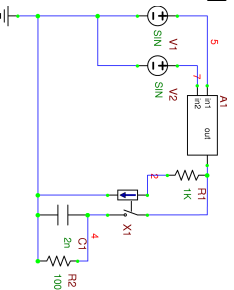
- V1*V2 = AM radio signal
- C1 & R2 ≈ earphone
- High impedance...
- Switch X1 = diode!
- "Voltage controlled"
- Perhaps a lousy switch
- Resistance(s) from plots
- $R = \Delta V / \Delta I = \text{slope}$
- Eyeball approximations



16e33

AM Demodulation

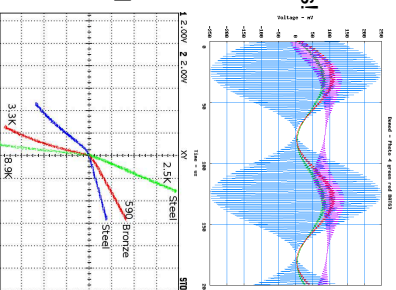
- Low voltage RF
- Remember: before tubes!
- Crystal diodes are OK
- Green ≈ 3.6 / 1 (rev/fwd)
- Red ≈ 5.6 / 1
- Modern diodes are NG
- Purple = Schottky ≈ ∞ / 1
- V_{fwd} much too high
- Bad diodes are good!



17e33

Iron Pyrite

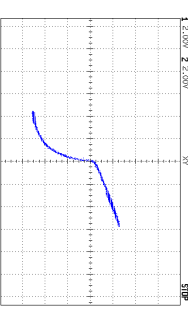
- Huh?
- Sorta Zener-ish
- Mostly OK diode
- For low I & V, anyway
- That's good enough!



18e33


Galena (?)

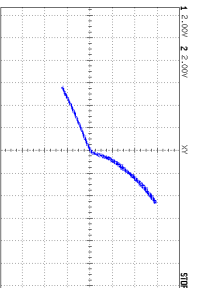- Backwards polarity
- Whatever that means
- Very low V_{fwd}
- Bronze probe
- So what?
- Best of many spots
- Who knew?
- Maybe it's just lead?




Chalcopyrite

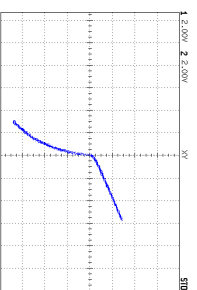- Say kai'•keh•pie'•right
- Looks diode-ish
- If you squint
- Moderate V_{fwd}
- Pretty good, actually
- But wait...




Chalcopyrite

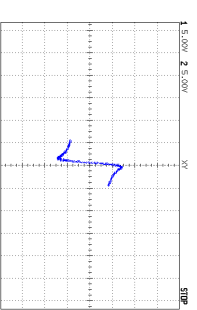- It's a Diaci
- Bilateral trigger diode
- It's a resistor!
- Very high resistance
- For very low current
- It's a *negative* resistor!!!
- Current ↑ with Voltage ↓
- Note scale change
- 5 V and 5 mA / div




Galvanized Steel

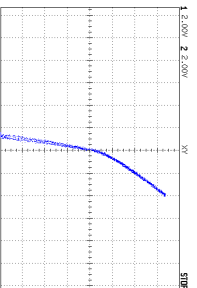- Propane torch
- Little black spots...
- Do this outdoors!
- Iron-tin-zinc alloy
- Cadmium? *ick!*
- Looks like high R
- And not a diode
- But wait...




Galvanized Steel Bestiary

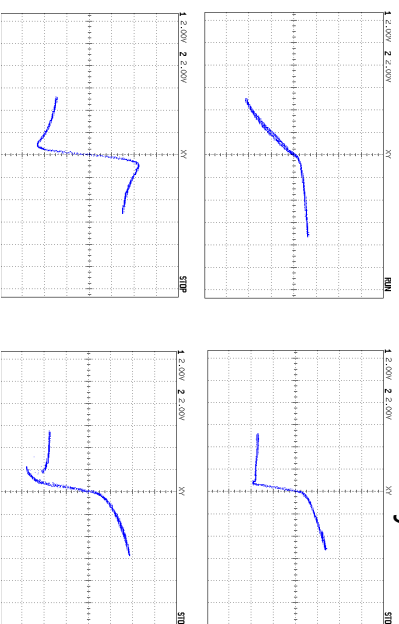


Steel Corrosion

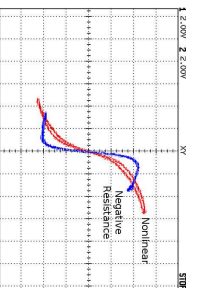- Nonlinear
- Symmetric
- Sorta, kinda
- Negative resistance
- Oscillator!
- No Battery Needed
- Self-biasing "circuit"
- DC bias + small AC



Linear Mixing Circuit

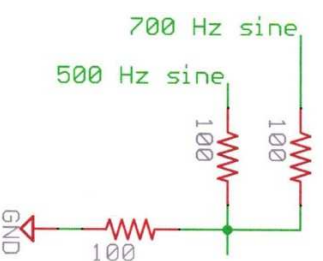- Only "resistors"
- Easy equations
- Ohm's Law, etc
- Sum of amplitudes
- No surprises




Rust Never Sleeps

- Ordinary steel bolt
- Salt + towel + copper
- Cu + Fe = 650 mV
- At *only* 1 mA
- Slow and steady
- AA cell
- 1500 mV & 10 mA
- 4 hours later...




Linear Mixing Results

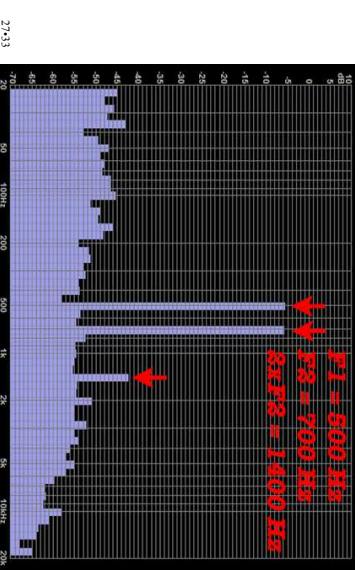


Nonlinear Mixing Circuit

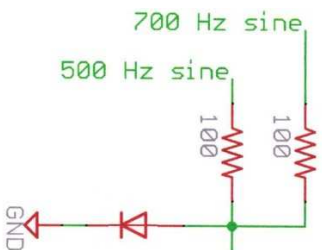- Usually a diode, but ...
- Any nonlinearity will do
- Equations? Hah!
- No analytic equations
- Simulation values?
- Harmonic frequencies
- $\pm nF_1 \pm mF_2$
- Surprises!



28x53

Nonlinear Mixing Results

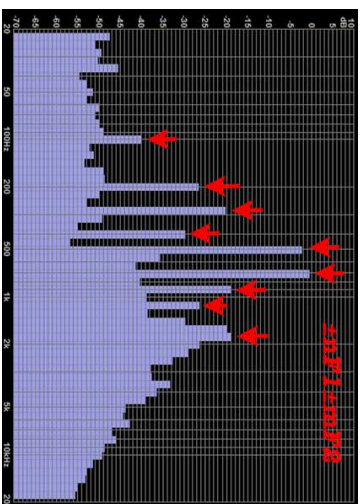

29x13

RF meets The Rusty Bolt

- Mountaintop radio
- Many transmitters
- High RF field intensity
- Sensitive receivers
- Galvanized towers
- Acid rain
- Corrosion happens
- Intermodulation!
- $\pm nF_1 \pm mF_2 \pm pF_3 \pm \dots$




MA Beacon NY - Photo by WB2UWU

30x53


DIY Diodes

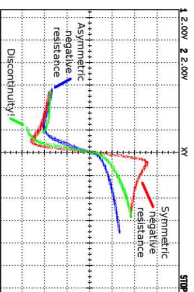- They're everywhere
- They're cheap
- OK, not that positioner
- They're easy, sorta
- You'll learn...
- ... about diodes
- ... about electronics
- ... about patience



31x53

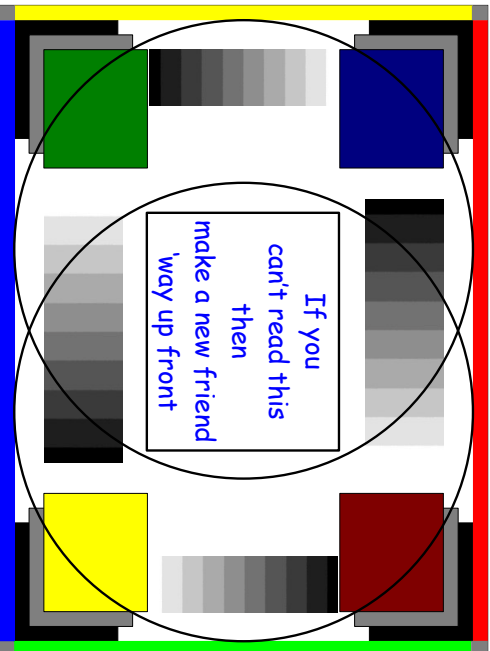If you
can't read this
then
make a new friend
'way up front



References

- My column in Circuit Cellar magazine: www.circuitcellar.com
- October 2006 has gritty details, has file of scripts, pictures, other stuff
- February & April 2003 describe nonlinear frequency mixing
- Semiconductor curve tracer using PC sound card: George Steber, WB9LVI
- Circuit Cellar, Jan 2004
- ARRL QEX, July 2006: www.arrl.org/qex/200607/qv/steber.pdf
- Good overview of crystal-set parameters: [www.oldradio.world.de/golun/analysis.htm](http://oldradio.world.de/golun/analysis.htm)
- Zinc negative resistance oscillators: <http://home.earthlink.net/~henryr/zincosc.htm>
- Galvanic Series table: www.ocean.udel.edu/seagrass/publications/corrosion.html
- Wood's metal, springs, phosphor bronze sheet, tools from MicroMark: <http://micromark.com>
- Taper pins and small parts from TimeSaver: www.timesavers.com
- Capturing oscilloscope traces with Kermit: www.columbia.edu/kermit/index.html
- Converting HPGL to bitmaps with hp2xx utility: www.gnu.org/software/hp2xx

32x13

Who Am I?

- Ed Nisley - KE4ZNU
- Say "NISS-lee", even though my ancestors were half-essed
- Engineer, author, tinker, family guy
- Circuit Cellar: Above the Ground Plane - www.circuitcellar.com
- Analog & RF stuff
- Digital Machinist: Along the G-Code Way - www.homeshopmachinist.net
- CNC machining & programming



Sept 02

33x53